


# Assignment 1 — FPGA Lab

EE22MTECH02005

January 2022
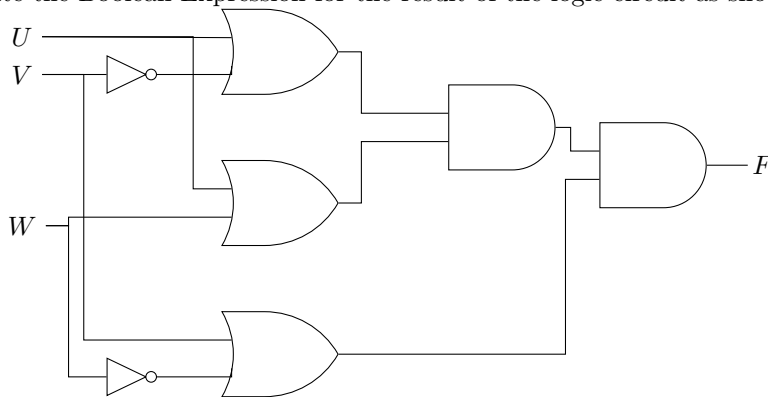
## 1 Question 1

Write the Boolean Expression for the result of the logic circuit as shown below:



## Solution

$$F = (U + \bar{V}).(U + W).(V + \bar{W}) = (U(V + \bar{W}))$$

---

## 2 Question 2

Implement the above using NAND logic.

## solution

$$F = U(V + \bar{W})$$

